

# Hidden Ground Loop Isolator


# Remove Center Console Panel





**Plug from  
Radio harness**

**5-Pin  
Connector**

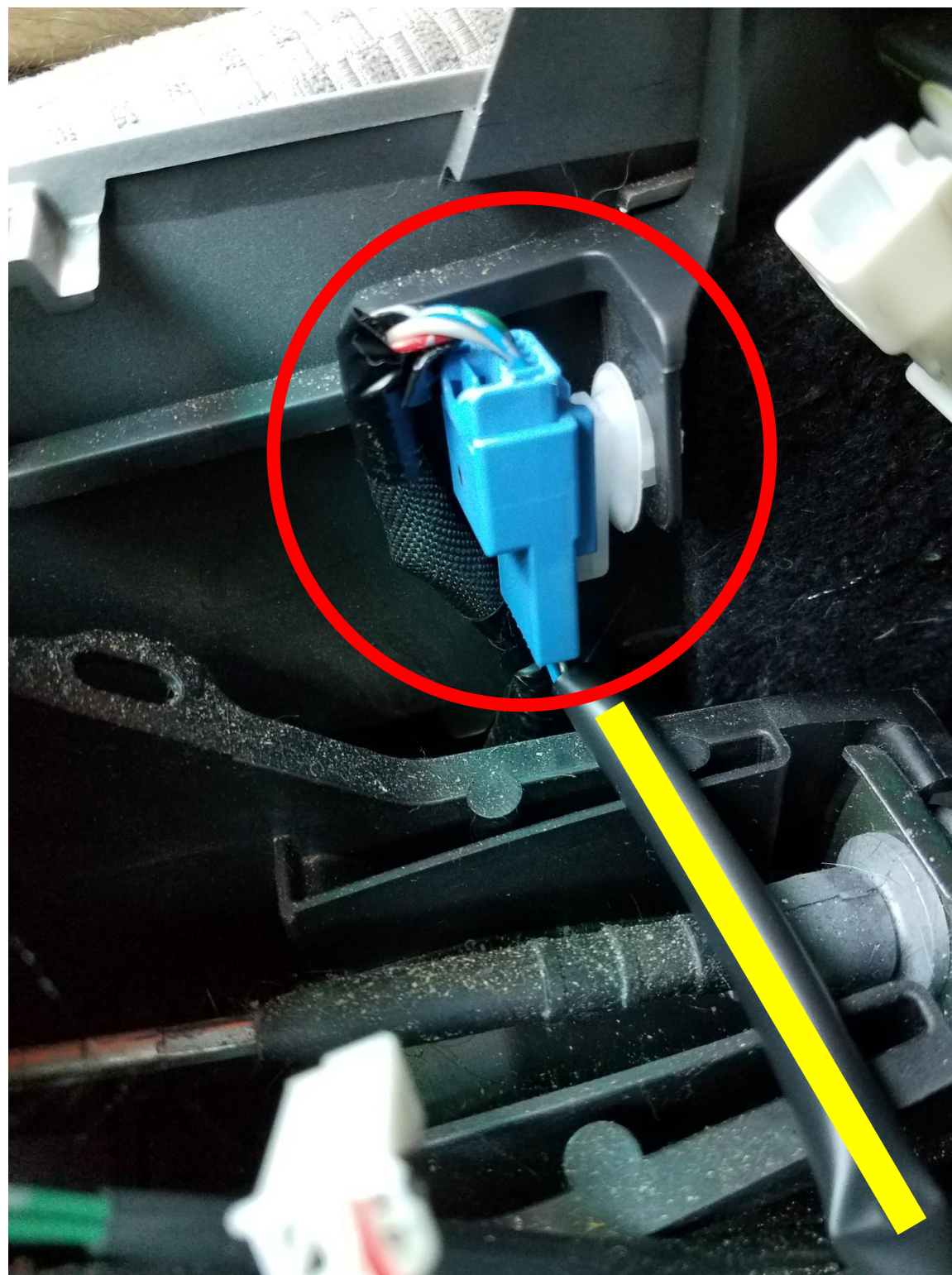

**Plug to 3.5mm  
jack in center  
console**

**4-pin  
connector**




**← Towards Radio      Towards Center Console →**



# Stock Wiring Harness


- Remove harness

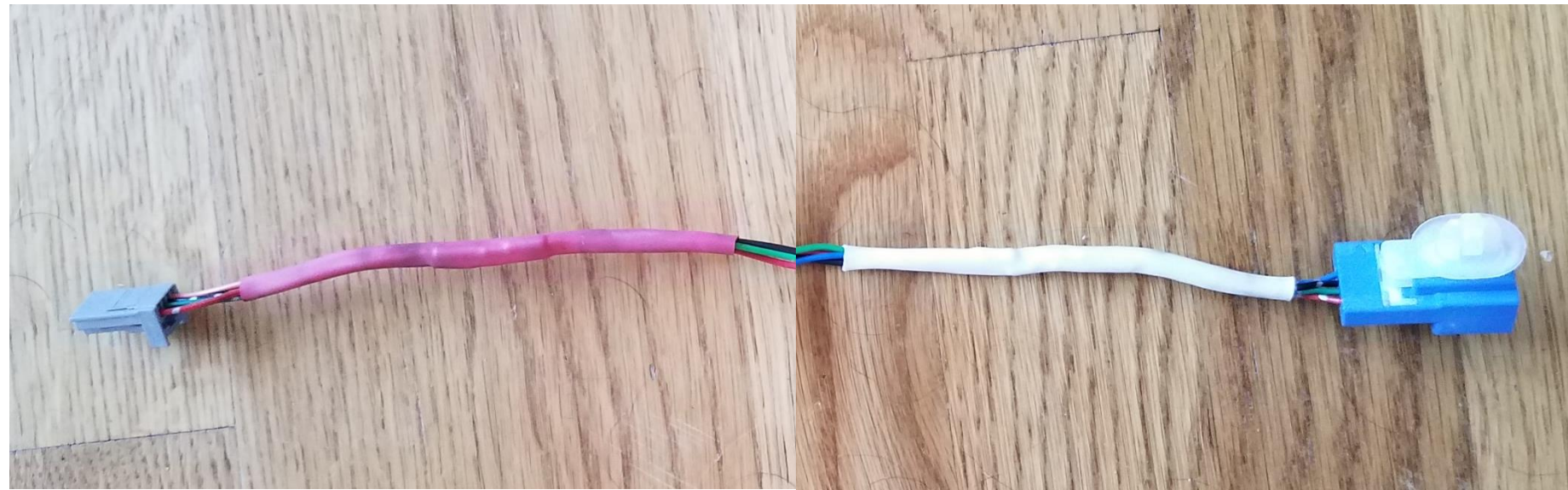

Create the Ground Loop Isolator
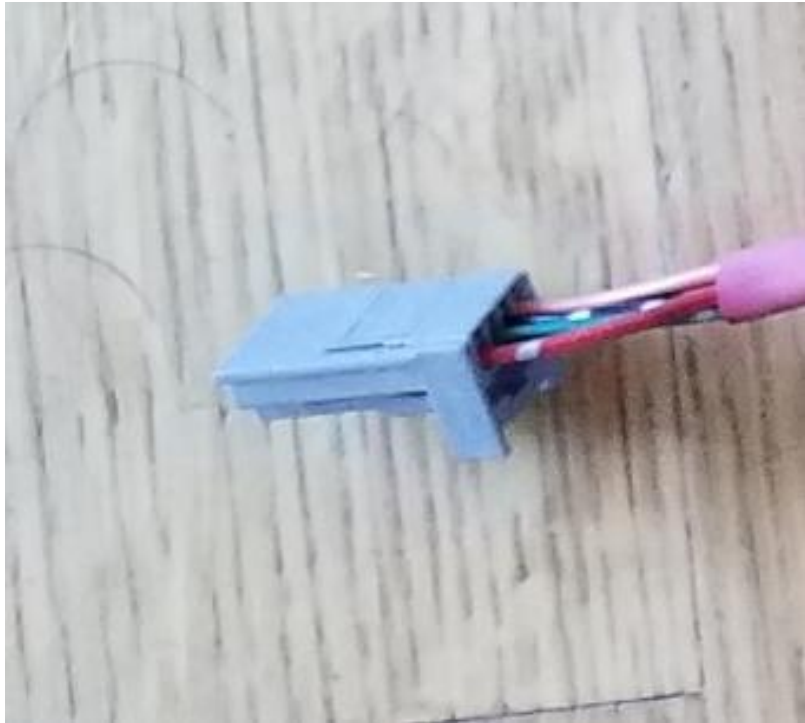
# Wiring Diagram


Cut all wires of the harness in the middle



Plug to 3.5mm jack in center console


4-pin connector

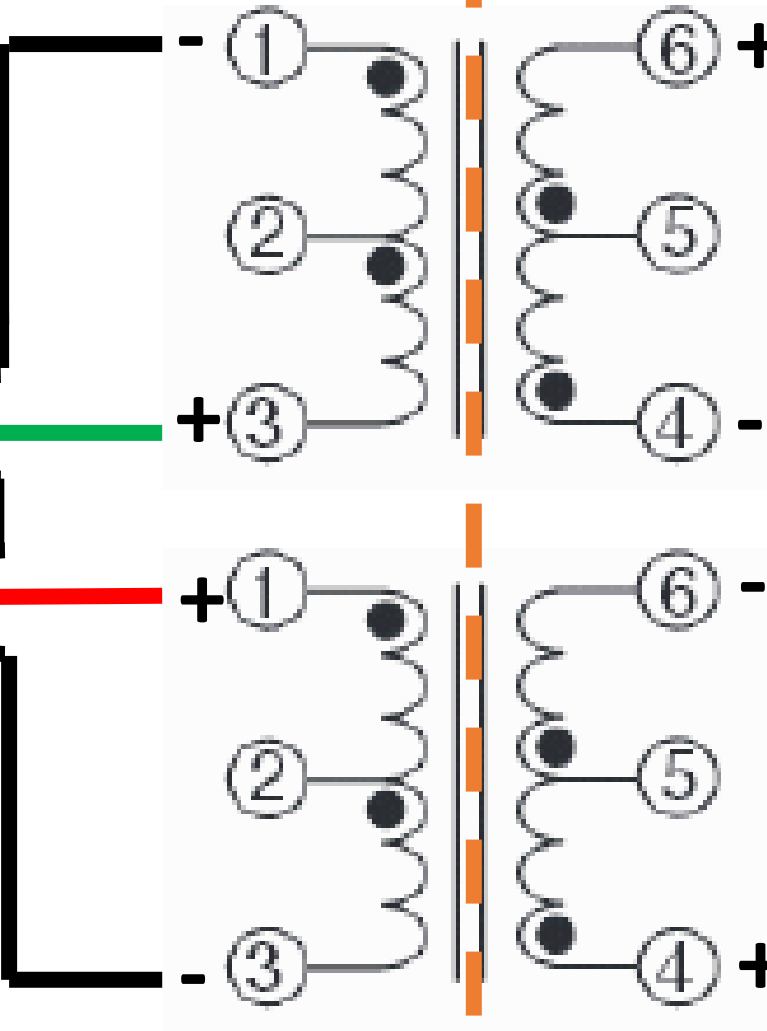Cut blue and connect to **NOTHING**, you no longer need it on this side of the harness



Connect blue to ground through R1 = 5.6k Ohm on this side of the harness

Pin Number	Color	Description
1	Red	Aux Left
2	Green	Aux Right
3	Black	Aux Ground
4	Blue	Aux Signal Switch
5	empty	N/A

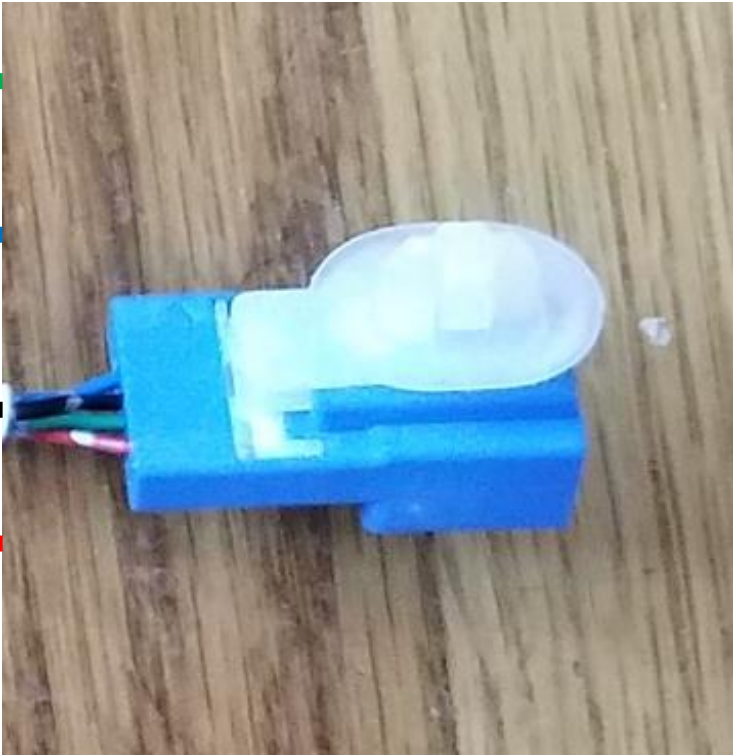



Plug from Radio harness

5-Pin Connector
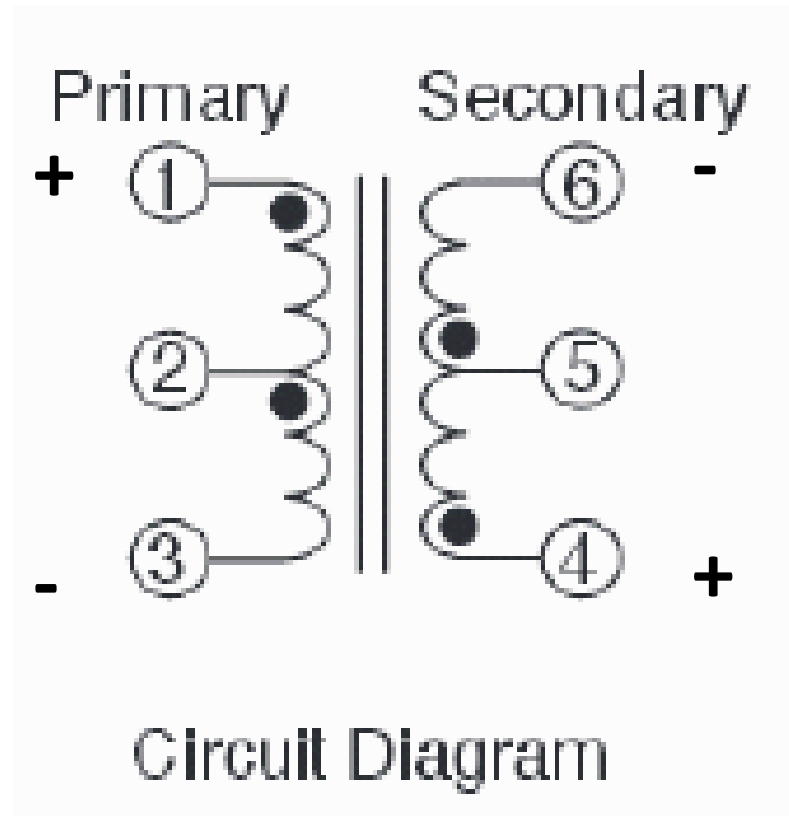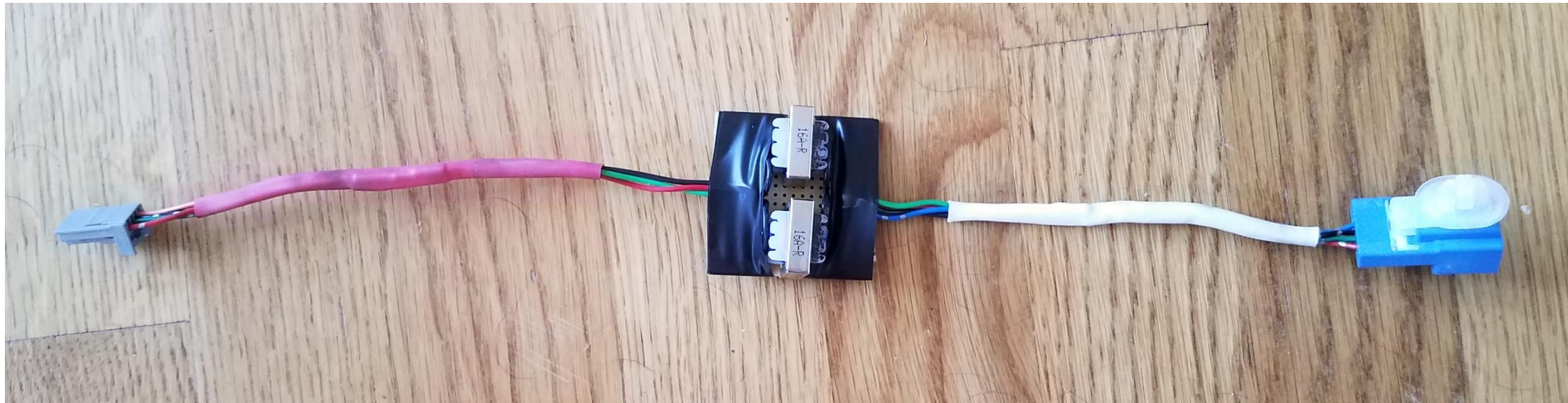
# Why used a 5.6k Ohm resistor?

- When using the stock, unaltered harness, the blue wire is used as a signal to switch to AUX. When a 3.5mm AUX cable is connected, the voltage in the blue line drops from 1.72 V to 0.6 V b/c the port switches the blue voltage across a 5.6k Ohm resistor.
- When you insert the Ground Loop Isolator into the circuit, you are essentially creating two separate circuits that are interacting via an electromagnetic field, therefore the OLD resistor in the switch no longer interacts with head unit blue wire.
- So you insert a NEW 3.5k Ohm resistor on the Head Unit side of the circuit to drop the voltage from 1.72 V to 0.6 V, tricking the Head Unit to think there is an AUX cable connected.





- Do not use the center pins (2 and 5) on the transformers, I cut them off
- Left and right channels have a common ground

2x Audio Transformers

- Model: Xicon 42TL016-R
- Ratio: 1:1
- Resistance: 600 Ohm

1x Printed Circuit Board

1x 5.6 Ohm Resistor

Wire, Solder, Soldering Iron



# Purchase Isolator Instead of Making One

PAC SNI-1/3.5 3.5-mm Ground Loop Noise Isolator



**I have not tested with this PAC ground loop isolator. Color combinations inside aux cords are varied from my audio, electrical experience.**

**Usually you will have red with white or red with black, with a copper braided shielding and possibly a foil shielding. (trim foil if it is present, no need to connect it to ground)**

**As long as you are consistent with your connections within your center console wiring harness, it will work.**



←      →  
**Towards Center Console (Male)**      **Towards Radio (Female)**



Color	Description
Red	Channel 1
White	Channel 2
Orange	Braided Copper Shielding
Grey	Foil Shielding (may or may not be present)

**Insert Ground Loop Isolator into the cut stock harness**

**Still need to connect blue wire from Head Unit side to through 5.6k Ohm resistor to ground on the Head unit side**